

Solid State Microwave Devices and Applications

Course Project

Power Amplifier Design



Group:

Harshul Agarwal	15D070043
Mohak Sahu	15D070047
Om Kolhe	150070008
Ritesh Kumar	15D070033



Design Steps

- Cascade the 2 stages and run S parameter simulation.


 


Fig: 2 stage amplifier

AIM :

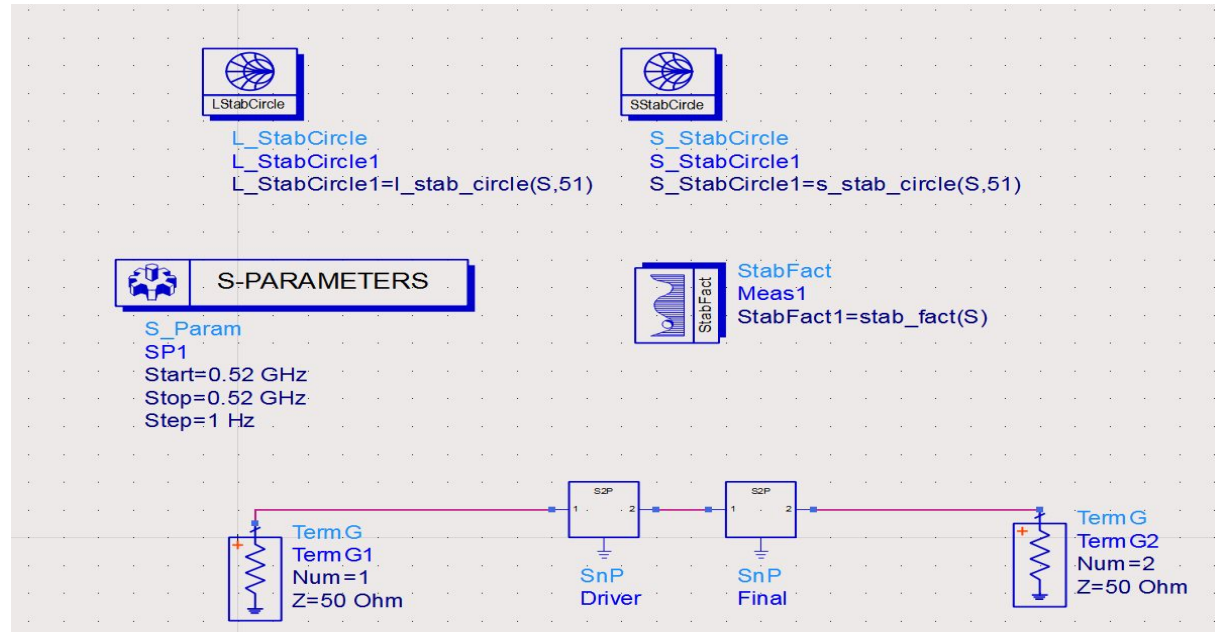- Get the combined S parameters.
- Check for stability.




S Parameter Simulation results :

freq	S(1,1)	S(1,2)	S(2,1)	S(2,2)
520.0 MHz	0.954 / -51.934	1.788E-4 / 12.589	10.175 / -175.692	0.734 / -135.415

Stability Factor :

freq	StabFact1
520.0 MHz	10.833

Stability Circles:

 

Observation:

- $K > 1$, $|\Delta| < 1$ means unconditional stability.
- Both source and load stability circles are outside the Smith chart

Conclusion : **We are safe**

Design Steps

Unilateral or Bilateral Design?

- S_{12} is not 0.
- Check unilateral figure of merit.

freq	U	Error_min_dB	Error_max_dB
520.0 MHz	0.031	-0.261	0.269

Observation: 0.27dB error is tolerable

Conclusion : We will do unilateral design

Design Steps

- Since we don't have stability issues, we can go with any possible gain.
- $G_{TU}(dB) = G_S(dB) + G_O(dB) + G_L(dB)$

AIM :

- Find maximum possible gain.
- Find the corresponding Γ_S and Γ_L

Equations :

$$\text{Eqn } G_{s_max} = 1/(1-(\text{mag}(S(1,1)))^2)$$

$$\text{Eqn } G_{o_max} = (\text{mag}(S(2,1)))^2$$

$$\text{Eqn } G_{L_max} = 1/(1-(\text{mag}(S(2,2)))^2)$$

$$\text{Eqn } G_{s_max_db} = 10 \cdot \log(G_{s_max})$$


$$\text{Eqn } G_{o_db} = 10 \cdot \log(G_{o_max})$$

$$\text{Eqn } G_{L_max_db} = 10 \cdot \log(G_{L_max})$$

freq	Gs_max	G_o	GL_max
520.0 MHz	11.057	103.524	2.167

freq	Gs_max_db	Go_dB	GL_max_db
520.0 MHz	10.436	20.150	3.358

 Design Step :Choosing Source and Load Gain




m3
indep(m3)=29
gs_circle3=0.936 / 52.327
gain=10.300, freq=520.0MHz
impedance = $Z_0 * (0.169 + j2.024)$

Eqn gs_circle1 = gs_circle(S, 8, 50)

Eqn gs_circle2=gs_circle(S, 5, 50)

Eqn gs_circle3=gs_circle(S, 10.3, 50)

 

m2
indep(m2)=45
gl_circle3=0.634 / 134.215
gain=3.200, freq=520.0MHz
impedance = $Z_0 * (0.262 + j0.397)$

Eqn gl_circle1=gl_circle(S, 2, 50)

Eqn gl_circle2=gl_circle(S, 2.5, 50)

Eqn gl_circle3=gl_circle(S, 3.2, 50)

Result :



- Source gain circle selected for Gain = 10.3dB
- Γ_s chosen for $Z_s = 50 * (0.169 + j2.024)$
- Load gain circle selected for Gain = 3.2 dB
- Γ_L chosen for $Z_L = 50 * (0.262 + j0.397)$

Design Step : Design matching network


Using **Smith Chart Utility** tool to match

source impedance : $50 * (0.169 + j2.024)$



Load impedance : $50 * (0.262 + j0.397)$

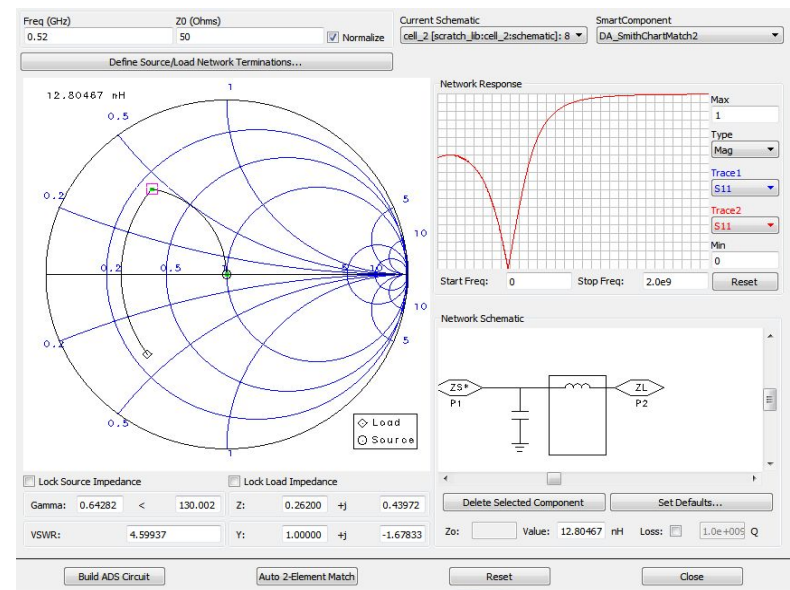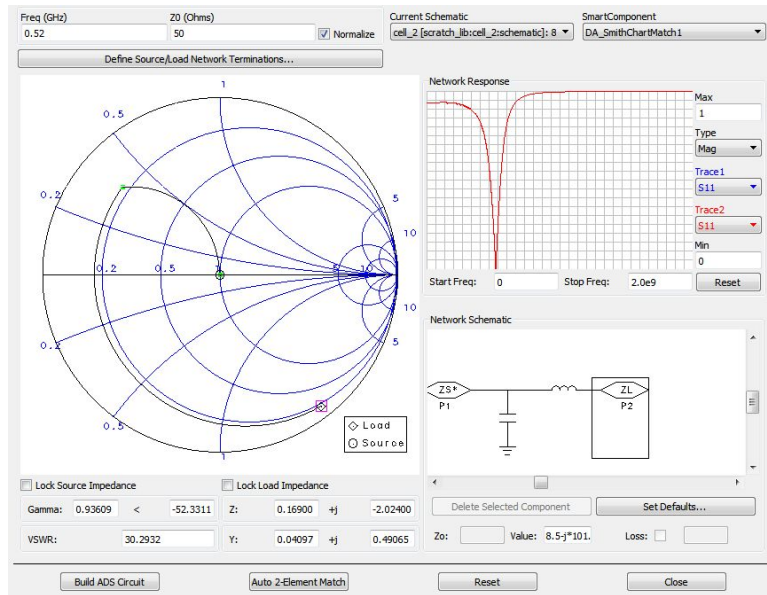

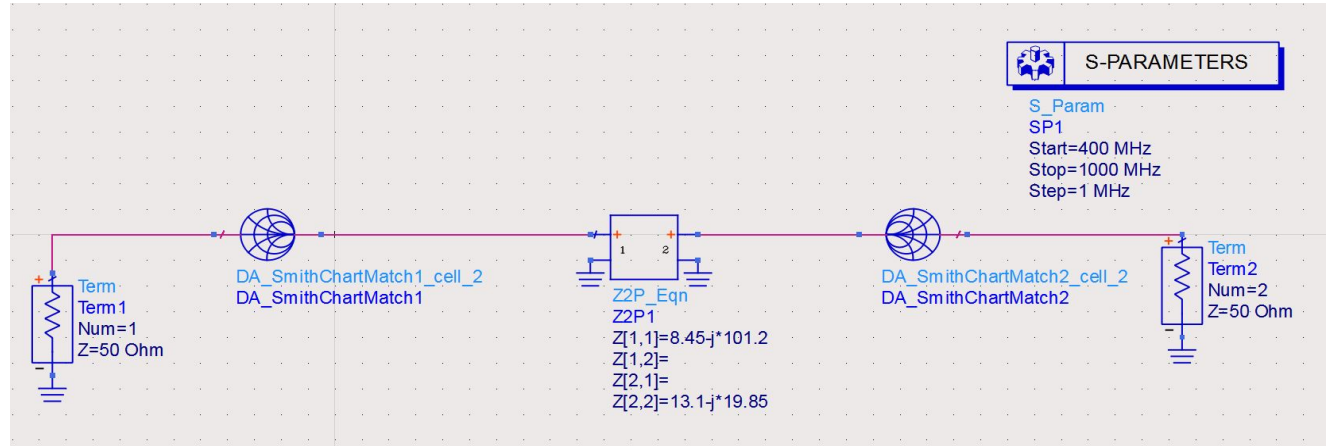
Matching simulation Setup (without the s param file):




Matching result :

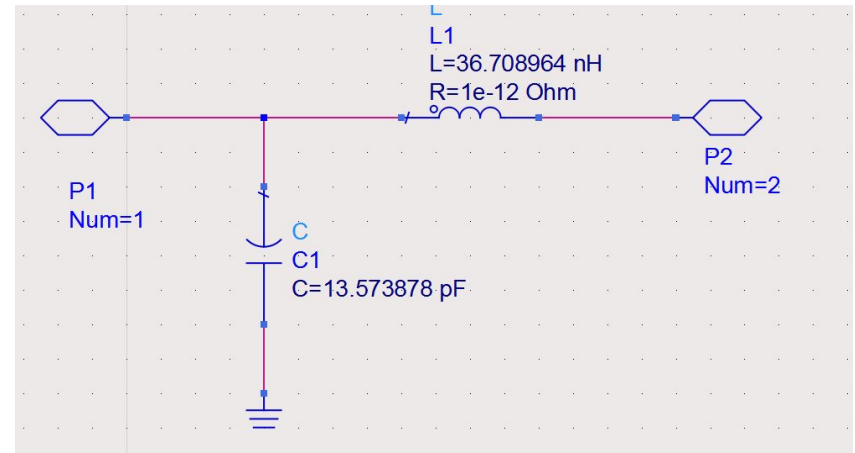 

Setup for simulation with S param file :

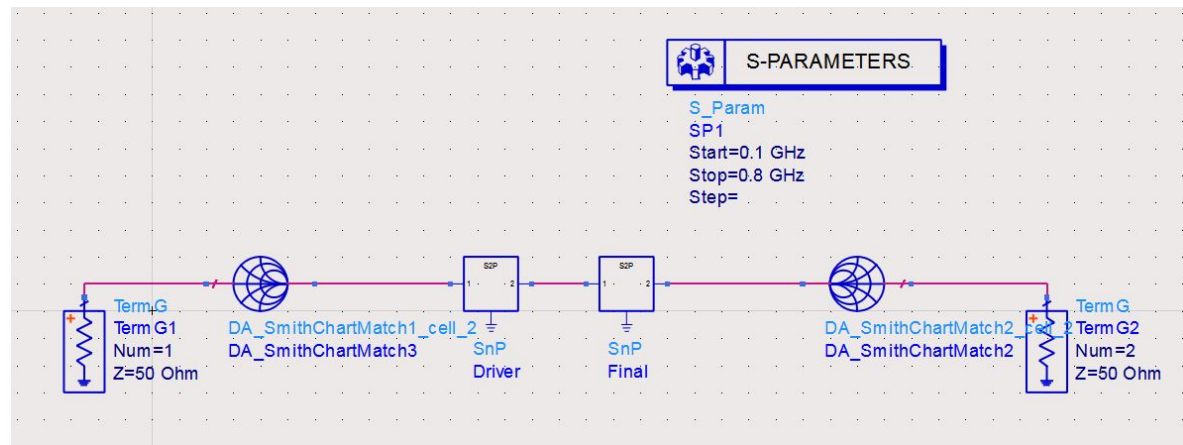

S param plot :

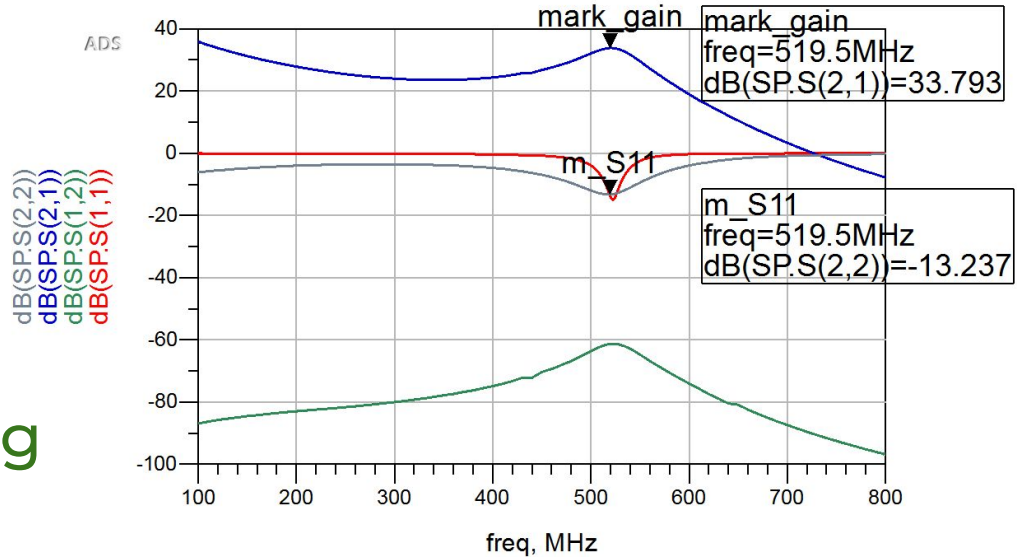

Conclusion : Working


Design Step : Bias T design and simulation

AIM :


- DC bias the transistor for proper working
- Separate DC and RF signals with proper blocking

Used capacitors for DC blocking and inductors for AC short

Simulation with transmission lines

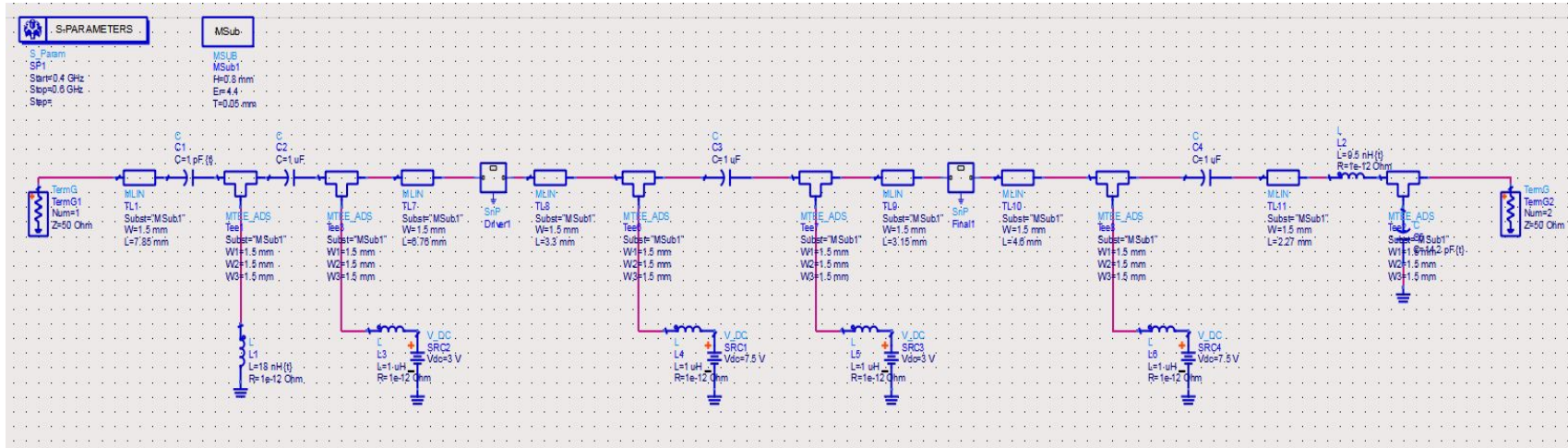

Simulation result :

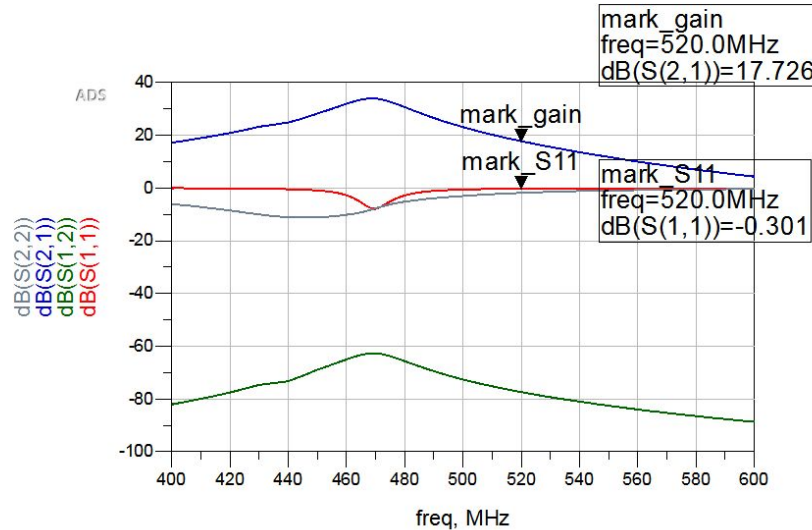


Observation:
Shift in peak frequency


Need to tune matching network elements to get the peaks at 520 MHz

Use tuner to tune L and C values of matching circuits


Tuner in ADS :

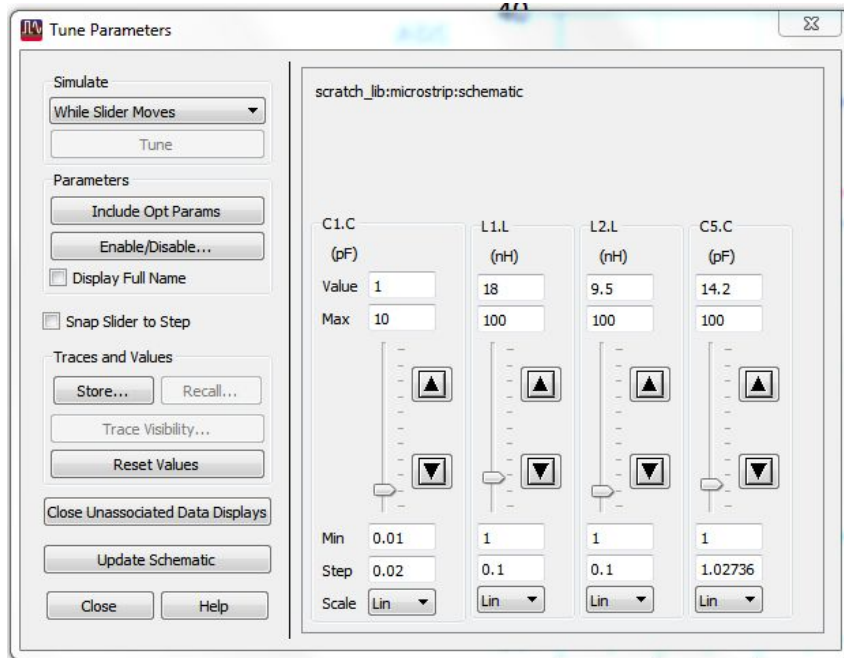


Final result after tuning :

 

Layout (in EAGLE):

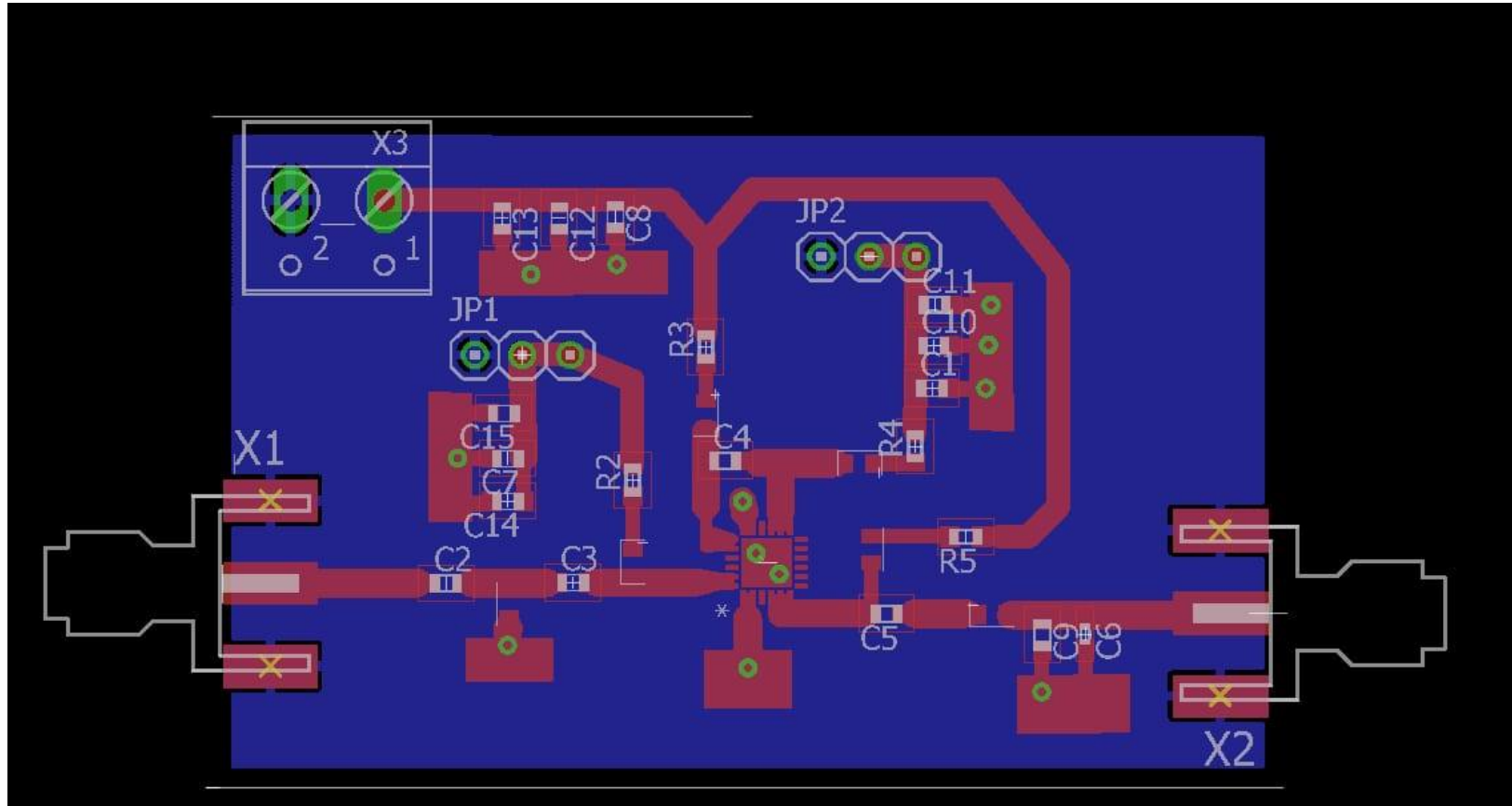

RESULT :

 

Observations:

- The DC part of circuit is functioning properly.
- At $V_{gs} = 3.3$ V and $V_{ds} = 5.4$ V the circuit is drawing 105 mA current.
- S_{21} observed -30DB

Improvements done during testing:

- Replaced 1uH inductor with 10uH (had better SRF) to avoid RF leaking into DC.
- Added 50 Ω resistors in the drain paths.